

# Digital Electronics

**Class 10**

**Lab Tutorial 19**

1. Create a truth table for this

