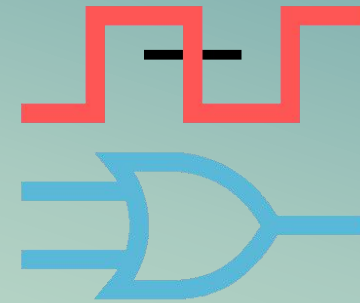


Digital Electronics

Class X
lab 20




Encoder




combinational circuit
that performs the
reverse operation of
Decoder

Inputs and Outputs for Encoder

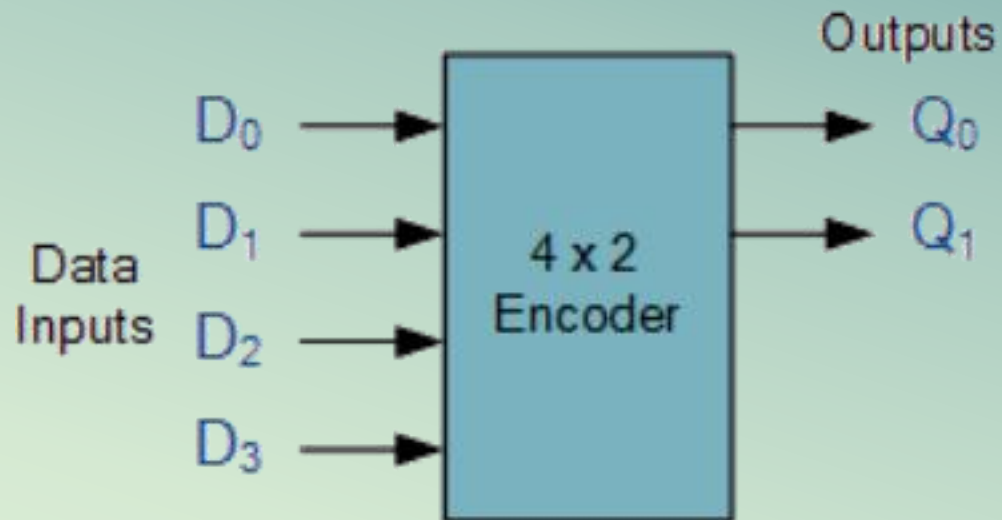

Inputs				Outputs	
D_3	D_2	D_1	D_0	Q_1	Q_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1
0	0	0	0	x	x

4 to 2 Encoder

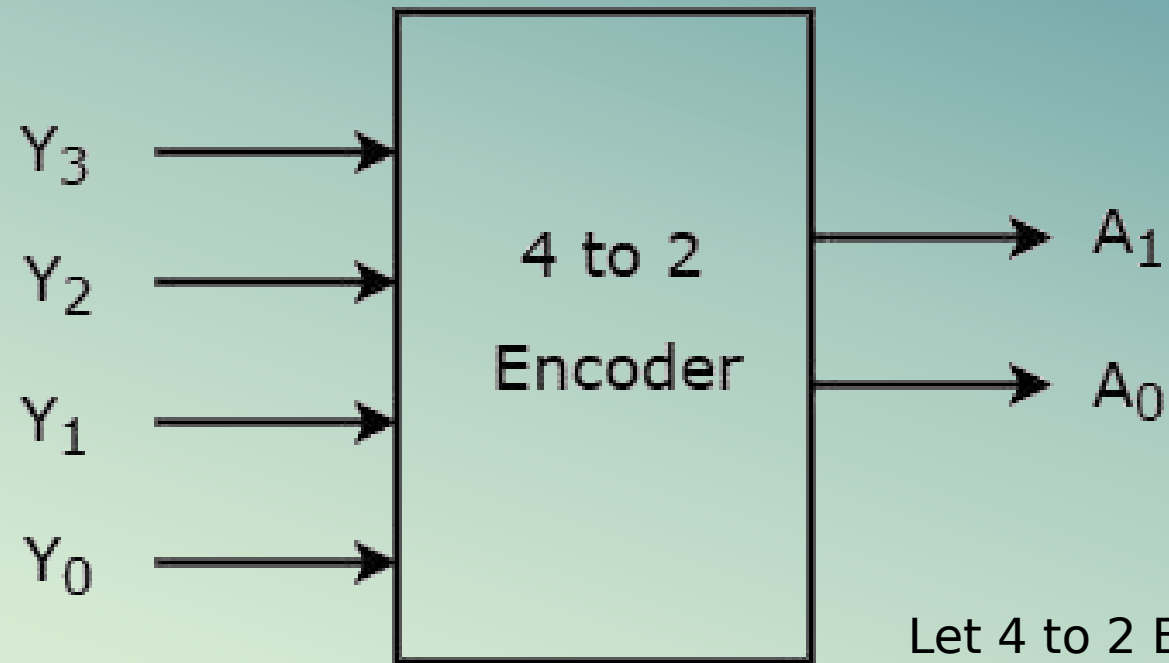


Let 4 to 2 Encoder has four inputs Y_3 , Y_2 , Y_1 & Y_0 and two outputs A_1 & A_0 . The block diagram of 4 to 2 Encoder is shown in the following figure

Truth table of 4 to 2 Encoder

Inputs				Outputs	
Y_3	Y_2	Y_1	Y_0	A_1	A_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

Octal to Binary Encoder

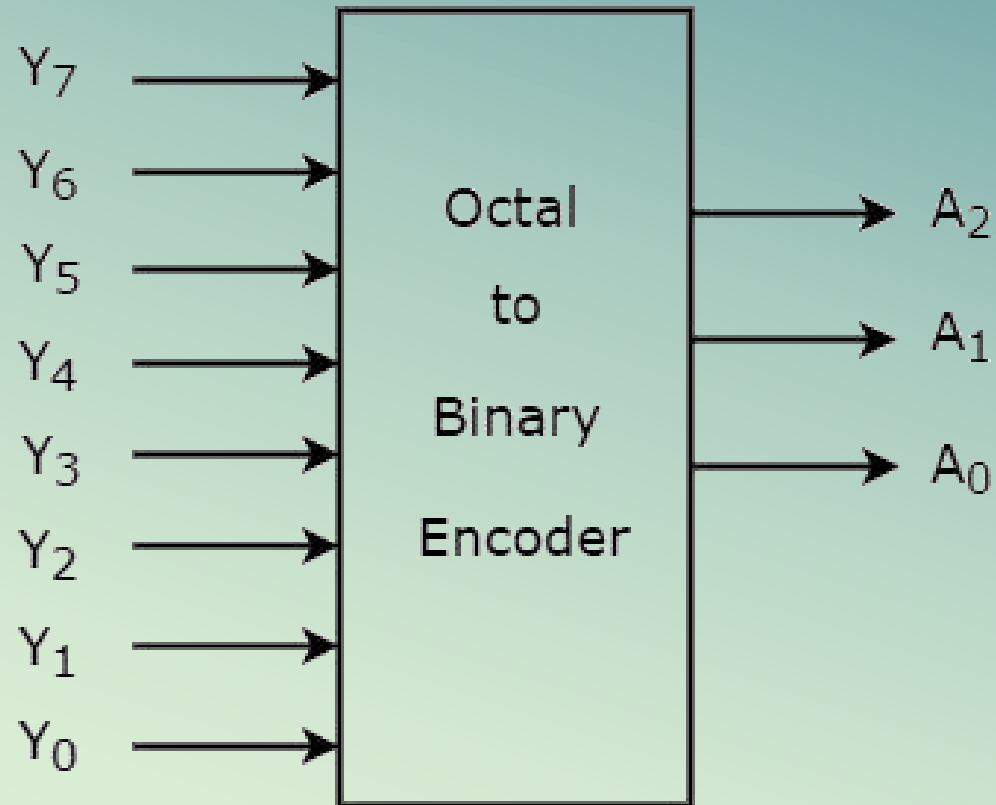

8 inputs and
3 outputs

Thank You