
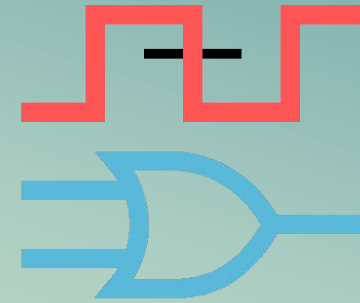


Digital Electronics

Class X
lab 19

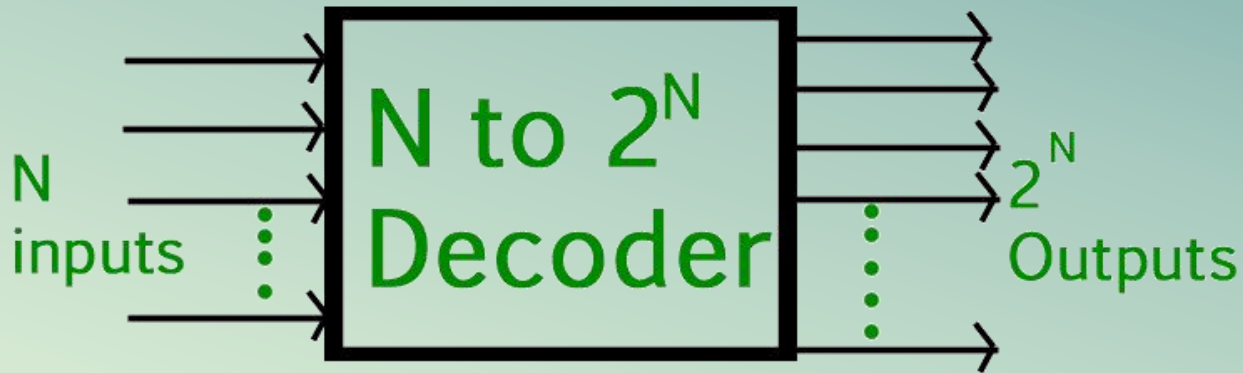

Decoder




Decoder is a combinational circuit that has 'n' input lines and maximum of 2^n output lines.

Input and Output for Basic Logic Gates


A	Y
0	1
1	0



A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

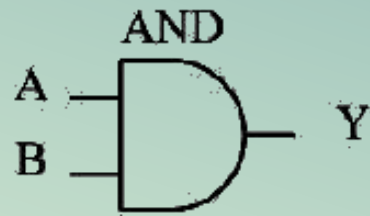


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

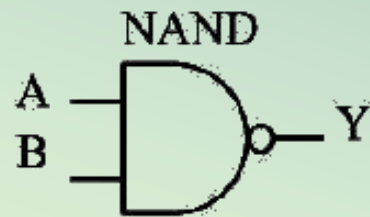

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0



A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

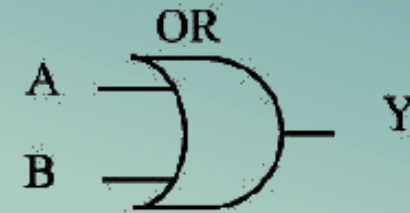

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0




Truth Table

A	B	AB
0	0	0
0	1	0
1	0	0
1	1	1

Truth table is a tabular representation of all the combinations of values for inputs and their corresponding outputs.

2 to 4 Decoder

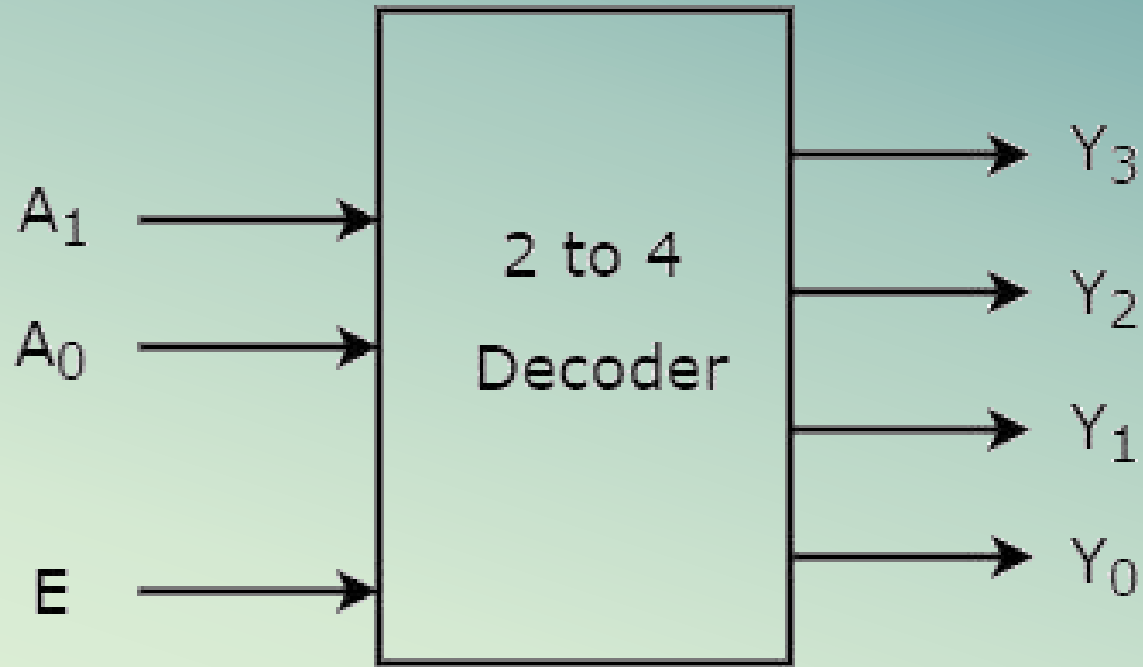


Let 2 to 4 Decoder has two inputs A_1 & A_0 and four outputs Y_3 , Y_2 , Y_1 & Y_0 . The block diagram of 2 to 4 decoder is shown in the following figure

Truth Table for 2 to 4 Decoder

Enable	Inputs		Outputs			
E	A ₁	A ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

2 to 4 Decoder Diagram

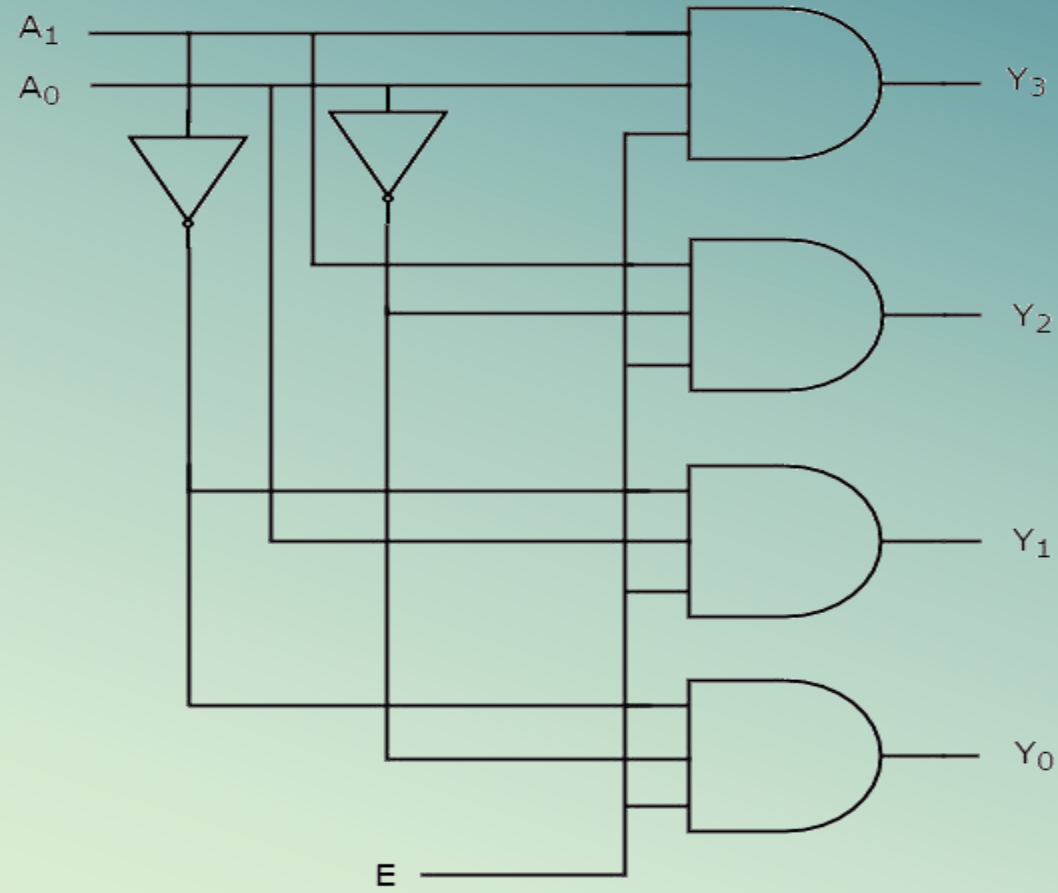

Thank You